

Name: Peter Muyang NI Class: AP Physics C ME/EM

姓名: 佺沐阳 班级: AP 物理 C 力学/电磁


目录

Current and the motion of Charges 电流与电荷运动.....	2
Resistance and Ohm's Law 电阻及欧姆定律.....	3
Energy in Electric Circuits 电路中的能量	4
Kirchhoff's Rules 基尔霍夫定律.....	6
Capacitance and RC Circuit 电容及 RC 电路.....	7

Peter Muyang Ni @ BNDS

Current and the motion of Charges 电流与电荷运动

Note

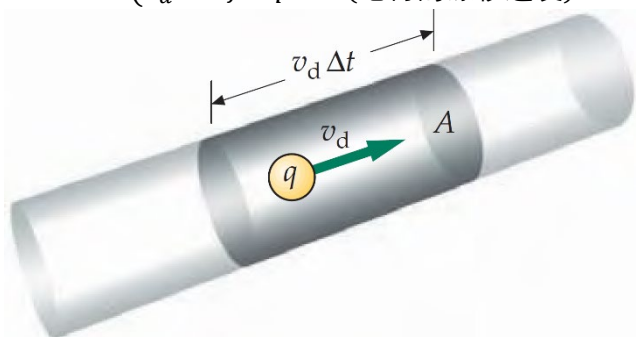初等数学	高等数学
$I = \frac{\Delta Q}{\Delta t}$	$I = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt}$
$\Delta Q = qnAv_d \Delta t$ $I = \frac{\Delta Q}{\Delta t} = qnAv_d$	
$\left\{ \begin{array}{l} n: \text{Number Density of particles} \\ q: \text{charge of each particle} \\ v_d: \text{drift speed (电荷的漂移速度)} \end{array} \right.$	
	
<p>The <u>current density vector</u>(<u>电流密度矢量</u>), \vec{j}, is specified by</p> $\vec{j} = qn\vec{v}_d$ <p>If \vec{j} is uniform and if the surface is flat, which means that \hat{n} would be uniform, then the flux can be expressed</p> $I = \int_S \vec{j} \cdot d\vec{A} = \vec{j} \cdot \vec{A} = JA \cos \theta$	

Example: In a certain particle accelerator, a current of 0.5mA is carried by a 5.0 MeV proton beam that has a radius equal to 1.5mm. The mass of a proton is $m = 1.67 \times 10^{-27} \text{ kg}$. The charge of a proton is $q = 1.60 \times 10^{-19} \text{ C}$.

注意：此处出现了新的能量单位 eV(电子伏特). 1 eV 是 1 个电子经过了 1V 的电势差后，所获得的能量。

(a) Find the number density of protons in the beam.

$$E_k = \frac{1}{2}mv^2 \Rightarrow v = \sqrt{\frac{2E_k}{m}}$$

$$I = qnAv \Rightarrow n = \frac{I}{qAv} = \frac{I}{qA} \sqrt{\frac{m}{2E_k}}$$

$$= \frac{0.5}{(1.60 \times 10^{-19})\pi(1.5 \times 10^{-3})^2} \sqrt{\frac{1.67 \times 10^{-27}}{2(5.0 \times 10^{-6})}} = 1.4 \times 10^{13} \left(\frac{\text{protons}}{\text{m}^3} \right)$$

(b) If the beam hits a target, how many protons hit the target in 1.0s?

$$\text{Total number } N = \frac{\Delta Q}{q}, \quad I = \frac{\Delta Q}{\Delta t}$$

$$\Rightarrow N = \frac{I\Delta t}{q} = \frac{0.5 \times 10^{-3}}{1.67 \times 10^{-19}} = 3.1 \times 10^{15} \text{ (protons)}$$

Resistance and Ohm's Law 电阻及欧姆定律

A segment of wire that has a current I . The potential drop $V_b - V_a$ is related to the electric field by:


$$V = V_b - V_a = E\Delta L$$

Resistance: the ratio of the potential drop.

$$R = \frac{V}{I}$$

SI unit: ohm (Ω)

$$1\Omega = 1V/A$$

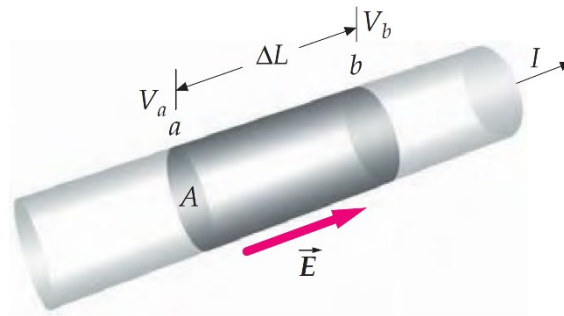

Ohmic Materials: Resistance does not depend on V or I

⇒ Fixed resistance material (in a wide range of conditions)


Ohm's Law:

$$V = IR$$


Resistance:

$$R = \rho \frac{L}{A}$$

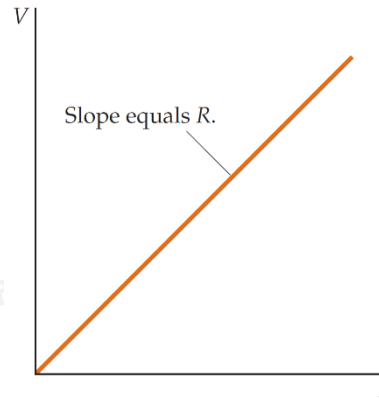(ρ : resistivity, L : length, A : cross-sectional area)



Resistivity ρ : depends on temperature

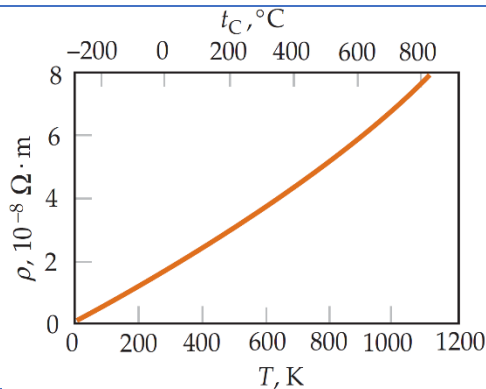

Example: Calculate the resistance per unit length of a 14-gauge copper wire: $\rho = 1.7 \times 10^{-8} (\Omega/m)$, diameter $d = 1.628 (mm)$ Area $A = 2.081 (mm^2)$.

$$R = \rho \frac{L}{A} = 1.7 \times 10^{-8} \frac{1}{2.081 \times 10^{-6}} = 8.2 \times 10^{-3} (\Omega)$$

Energy in Electric Circuits 电路中的能量

$$-E_p = \Delta Q(V_a - V_b) = \Delta QV$$


$$-\frac{dE_p}{dt} = \frac{dQ}{dt}V = IV$$

Rate of Potential Energy Loss

(Power 功率):

$$\Rightarrow P = IV$$

$$P = IV = I^2R = V^2/R$$

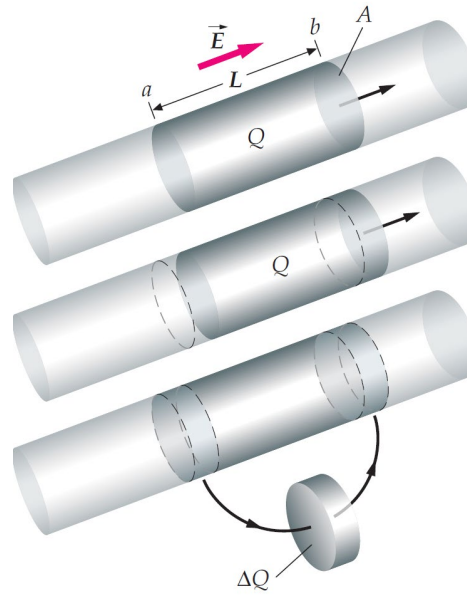

Example: The rated current of an ear-piece is 10mA and the equivalent resistance of it is 50 Ω. Determine the working power and rated voltage of it.

$$P = I^2R = 0.01^2 \times 50 = 5 \times 10^{-3} \text{ (W)} = 5 \text{ (mW)}$$

$$P = IV \Rightarrow V = P/I = (5 \times 10^{-3}) / (10 \times 10^{-3}) = 0.5 \text{ (V)}$$

Battery 电池:

An ideal battery is a source of energy that maintains a constant potential difference between its two terminals (independent of current through the battery).


The work per unit charge it provided is called ϵ (electromotive force 电动势)

$$P = \frac{\Delta Q}{\Delta t} \epsilon = I\epsilon$$

(功率 = 电流 · 电动势)

$$V_a - V_b = IR = \epsilon \Rightarrow I = \frac{\epsilon}{R}$$
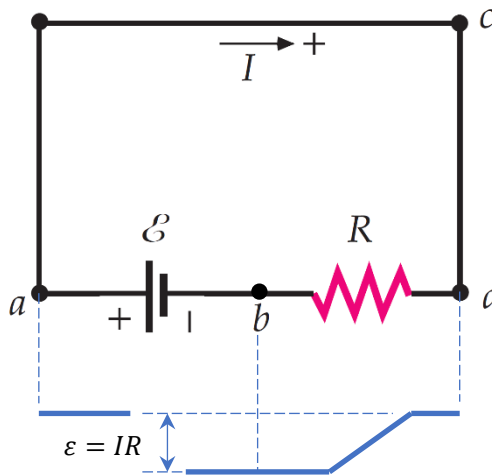
$$E = Q\epsilon \text{ (能量 = 电荷量 · 电动势)} \quad I = \Delta Q / \Delta t$$



A real battery consists of an ideal battery and an internal resistance r .

$$V_a - V_b = IR = \epsilon - Ir$$

$$\Rightarrow I = \frac{\epsilon}{R + r} \text{ 或 } \epsilon = Ir + IR$$

Example: A small bulb of 11Ω is connected across a battery of 36 V and internal resistance 1Ω. Find

a. the current

$$I = \frac{\varepsilon}{R + r} = \frac{36}{11 + 1} = 3 \text{ (A)}$$

b. the terminal voltage of the battery

$$V_a - V_b = IR = 3 \times 11 = 33 \text{ (V)}$$

c. the power supply by the chemical reactions

$$P = I\varepsilon = 3 \times 36 = 108 \text{ (W)}$$

d. the power delivered to the bulb.

$$P = I^2R = 3^2 \times 11 = 99 \text{ (W)}$$

e. the power consumed by the internal resistance.

$$P = I^2r = 3^2 \times 1 = 9 \text{ (W)}$$

f. If the battery is rated at $15 \text{ A} \cdot \text{h}$, how much energy does the battery store?

$$1 \text{ h} = 3600 \text{ s}$$

$$E = Q\varepsilon = (I\Delta t)\varepsilon = 15 \times 3600 \times 6 = 3240 \text{ (J)}$$

思考下面这样计算能量为什么不对?


$$E = Pt = 108 \times 3600 = \dots$$

Example: For a battery that has an emf equal to ε and internal resistance equal to r , what value of external resistance R should be placed across the terminals to obtain the maximum power delivered to the resistor?

$$I = \frac{\varepsilon}{R + r}$$

$$P = I^2R = \frac{\varepsilon^2 R}{(R + r)^2}$$


$$\frac{dP}{dR} = 0 \Rightarrow R = r$$

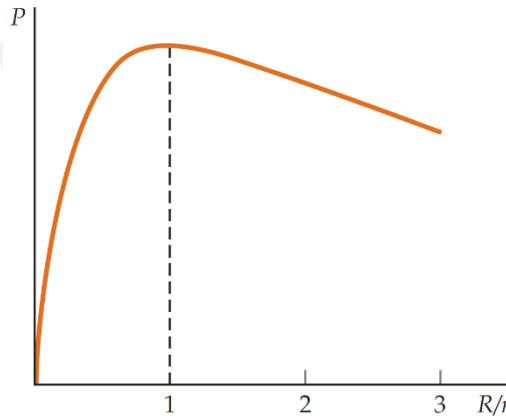

Resistors in Series(串联电阻)

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$


- 串联电路中电流 I 处处相等
- 串联电路总电压是各个分电压之和

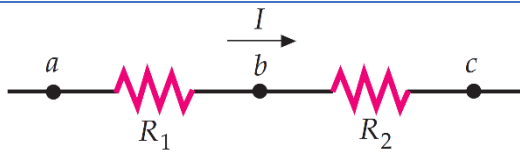

Resistors in Parallel(并联电阻)

$$1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3 + \dots$$

- 并联电路两端电压 V 相等
- 并联电路总电流是各个分电流之和

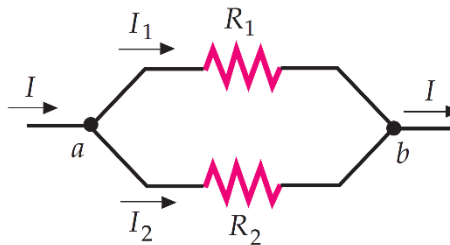

Kirchhoff's Rules 基尔霍夫定律

Note

- 1 The node rule: $I_{in} = I_{out}$
- 2 The loop rule: closed loop \Rightarrow Potential Difference be 0

解题步骤:

1. 找到 node
2. 找到 loop


解题关键:

- 1 正负号: 电池正负极不要搞错。
- 2 正负号: 电流方向不要搞错, 沿电流方向电压升高还是降低不要搞错。

Example For the circuit in the right figure, which of the following is true?

- (A) $V_B - V_A = -2V$
 (B) $V_B - V_A = +3V$
 (C) $V_B - V_A = -3V$
 (D) $V_B - V_A = -5V$
 (E) $V_B - V_A = +5V$


Barron 14-5 答案(B)

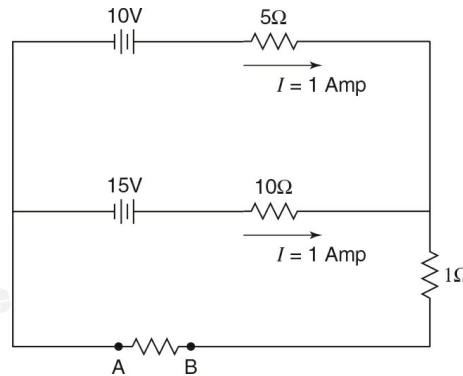

Example In the right, if the potential at point A is chosen to be zero, what is the potential at point B?

- (A) +1V
 (B) -1V
 (C) +2V
 (D) -2V
 (E) +3V

Barron 14-10 答案(A)

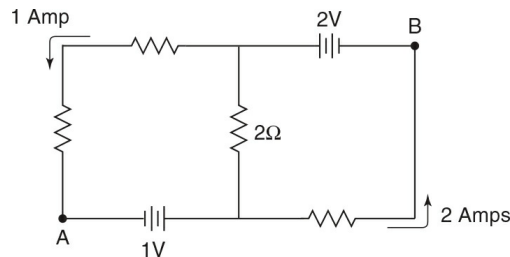

Capacitance and RC Circuit 电容及 RC 电路

Note

- Capacitance: $C = Q/V$
Isolated spherical conductor $C = 4\pi\epsilon_0 R$
Parallel-plate capacitor $C = \epsilon_0 A/d$
- Energy in Capacitors: $dU = VdQ = QdQ/C \Rightarrow U = \int \frac{Q}{C} dQ = \frac{Q^2}{2C}$
 $U = \frac{1}{2}QV = \frac{1}{2}\frac{Q^2}{C} = \frac{1}{2}CV^2$
- Dielectrics: $C = kC_0$ $\epsilon = k\epsilon_0$
 $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$
- Equivalent Capacitance:
Parallel capacitors $C_{eq} = C_1 + C_2 + C_3 + \dots$
Series capacitors $1/C_{eq} = 1/C_1 + 1/C_2 + 1/C_3 + \dots$


对比

电容: $U = \frac{1}{2}QV = \frac{1}{2}\frac{Q^2}{C} = \frac{1}{2}CV^2$

电阻: $P = IV = \frac{V^2}{R} = I^2R$

Example When the circuit shown in the right figure has reached a steady state, what is the charge on capacitor 1 (which has a capacitance C_1 , as shown)?

- (A) $C_1^2 V / (C_1 + C_2)$
 (B) $C_1 C_2 V / (C_1 + C_2)$
 (C) $C_2^2 V / (C_1 + C_2)$
 (D) $C_1 V$
 (E) $\frac{1}{2} C_1 V$

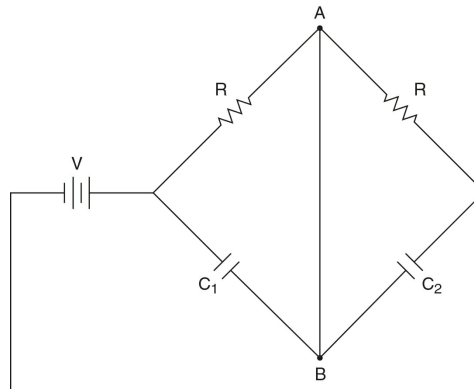

Barron 15-9 答案(E)


Discharging a capacitor through a resistor

$$\begin{cases} V_C = V_R \\ I(t) = -\frac{dQ}{dt} \\ I_0 = \frac{V_0}{R} = \frac{Q_0}{RC} \end{cases}$$

$$V_C = V_R \Rightarrow \frac{Q}{C} = IR = -\frac{dQ}{dt} R$$

$$Q(t) = Q_0 e^{-\frac{t}{RC}}$$
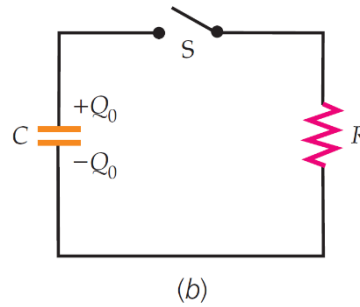
$$I(t) = -\frac{dQ}{dt} = \frac{Q_0}{RC} e^{-\frac{t}{RC}} = I_0 e^{-\frac{t}{RC}}$$




Charging a capacitor

$$\begin{cases} \mathcal{E} = V_R + V_C = IR + Q/C \\ I(t) = +\frac{dQ}{dt} \\ I_0 = \frac{\mathcal{E}}{R} = \frac{Q_0}{RC} \end{cases}$$

$$\mathcal{E} = IR + \frac{Q}{C} = \frac{dQ}{dt} R + \frac{Q}{C}$$

$$Q(t) = Q_{final} \left(1 - e^{-\frac{t}{RC}}\right) \quad Q_{final} = C\mathcal{E}$$

$$I(t) = I_0 e^{-\frac{t}{RC}}$$

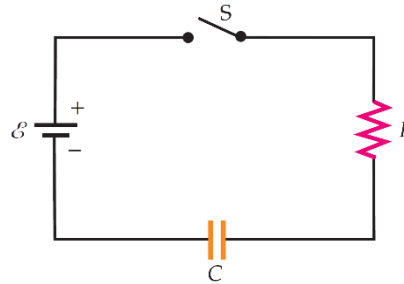


Time constant

$$\tau = RC \text{ (second)}$$

图示电路在开关闭合时充电，开关断开时放电。分析在充电和放电时的时间常数,初始电流。

Barron 16-9

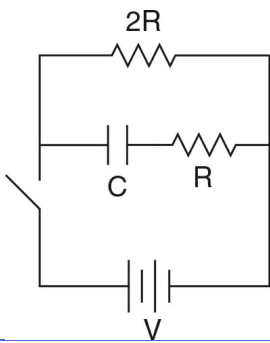


Charging: $\tau = RC$
Discharging: $\tau = 3RC$

Charging: $I_0 = \frac{V}{R}$

Discharging: $I_0 = \frac{V}{3R}$

寒假作业 Question 24


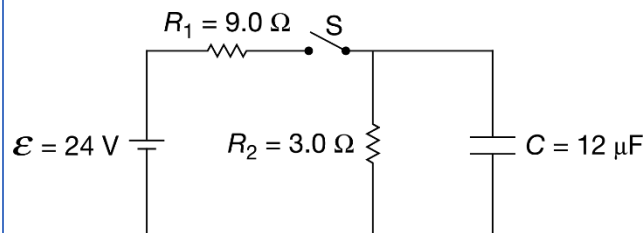


Charging: $\tau = (9\Omega)(12\mu F) = 108 (\mu s)$
Discharging: $\tau = (3\Omega)(12\mu F) = 36 (\mu s)$

Charging: $I_0 = \frac{\mathcal{E}}{R} = \frac{24}{9} = \frac{8}{3} (A)$

Discharging: $I_0 = \frac{V}{R} = \frac{6}{3} = 2 (A)$

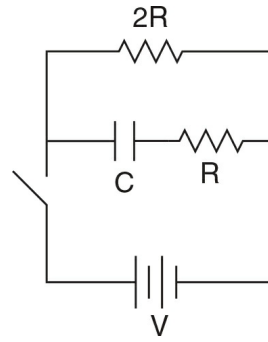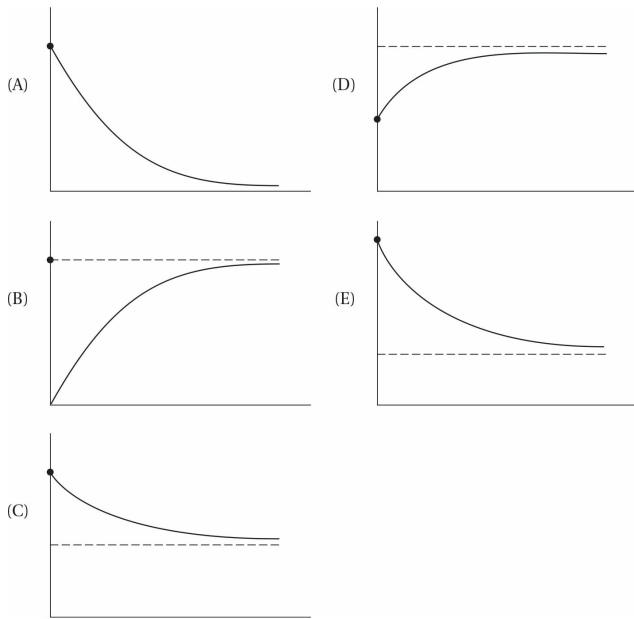Barron 16-9: For the circuit in the right figure, which of the graphs in Figure 16.7 shows the current through the battery as a function of time?




答案(E)

Peter Muyang Ni @ BNS

寒假作业 Question 24

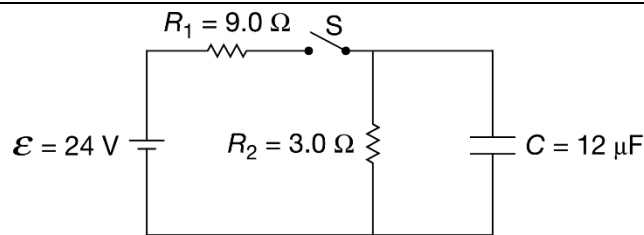A power supply is set to $\mathcal{E} = 24V$ and is connected to resistors $R_1 = 9.0\Omega$ and $R_2 = 3.0\Omega$, capacitor $C = 12\mu F$, and switch S , as shown in the figure. Initially, the capacitor is uncharged, and switch S is open.



(a) At time $t=0$, the switch is then closed.

i. Calculate the current through R_1 immediately after the switch is closed.

After the switch is closed, the capacitor branch is short.

The current through R_1 is $I_1 : I_1 = \mathcal{E} / R_1 = 24/9 = 8/3$ (A)

ii. Determine the current through R_2 immediately after the switch is closed.

As the capacitor branch is short, the voltage across C and R_2 is equal 0.

The current through R_2 is $I_2 : I_2 = 0/3.0 = 0$ (A)

A long time after the switch is closed, the circuit reaches steady-state conditions.

(b) Calculate the potential difference across R_2 .

A long time after the switch is closed, the circuit reaches steady-state conditions so that the current through C is 0 and the voltage across C equals to the potential difference across R_2 .


$R_{12} = R_1 + R_2 = 12$ (Ω)

The voltage across R_2 is $V_2 : V_2 / \mathcal{E} = R_2 / R_{12} \quad V_2 = 6$ (V)

(c) Calculate the magnitude of the charge Q on the positive plate of the capacitor.

$Q = V * C = 6 * 12 = 72$ (μC)

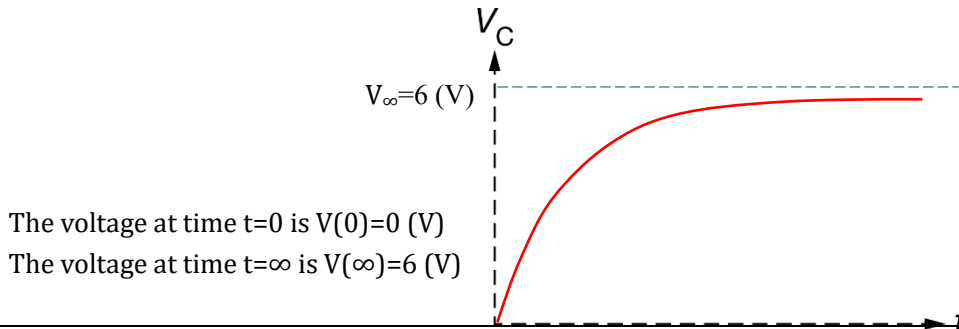(d) On the axes shown, sketch a graph of the potential difference V_C across the capacitor as a function of time t . Explicitly label any intercepts, asymptotes, maxima, or minima with values or expressions, as appropriate.




After steady-state conditions are reached, the switch is now opened, and time is reset to $t=0$.

(e) Using integral calculus, derive an expression for the charge $q(t)$ on the capacitor as a function of time t after the switch is opened. Express your answer in terms of Q_0 .

After the switch is opened, the capacitor will discharge through resistor R_2 .

$$q(t) = Q_0 e^{-\frac{t}{RC}} \text{ where } Q_0 = 72 \mu\text{C}, C=12 \mu\text{F}, R=R_2=3.0 \Omega.$$

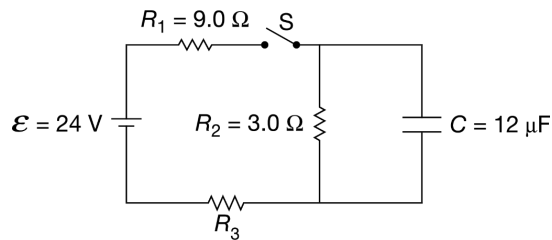The capacitor is discharged, and a third resistor is added to the circuit, as shown above. The switch is then closed.



(f) Does the time it takes for the charge on the capacitor to reach $2/3$ of its maximum value increase, decrease, or stay the same as compared to the circuit in part (a)?

Increase Decrease Stay the same

Justify your answer.

As total resistance is increased after the new resistor is inserted, according to the charging equation:

$$Q(t) = Q_0 e^{-\frac{t}{RC}}$$

Where R is increased. So that the time it takes for the charge on the capacitor to reach $2/3$ of its maximum value would increase.

Increase